

**VHDL Code
Simulation & Implementation
in ISE Xilinx**


UART Controller:

**UART_RX / RAM_1024X8 / UART_TX
UART_RX_TB**

Mohammad Niknam

Block Diagram:

UART_Controller

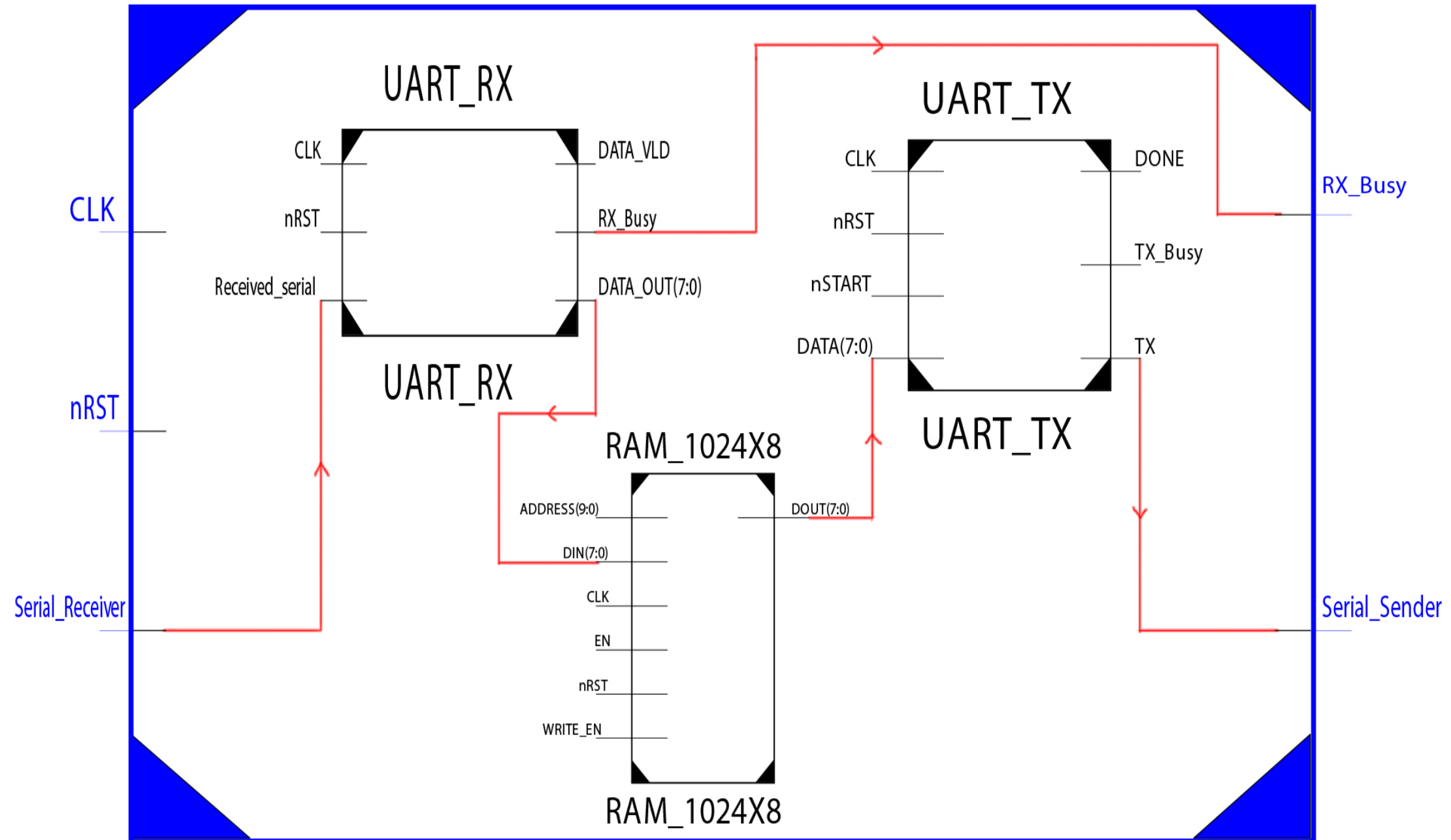

ماژولی با عملکرد زیر را طراحی و مبتنی بر VHDL سنتزپذیر توصیف نمایید:

ورودی سریال بر اساس استاندارد UART را دریافت کرده و به ترتیب در یک حافظه با ظرفیت یک کیلو بایت (1024 بایت) ذخیره می کند. پس از تکمیل ظرفیت حافظه (دریافت 1024 بایت ورودی یا همان 1024 بسته داده) این بار مقادیر نوشته شده در حافظه بر اساس استاندارد UART ارسال می شوند. پس از ارسال تمامی داده های حافظه، ماژول دوباره در وضعیت دریافت اطلاعات قرار می گیرد (پیشنهاد میشود، خروجی برای اعلان وضعیت فعلی ماژول در نظر بگیرید).

(راهنمایی: پیش از این هر سه ماژول اصلی شامل کنترلر دریافت و ارسال UART و همچنین حافظه را توصیف کرده ایم. پس کافی است که این ماژول ها به درستی جایگذاری شوند و یک ماشین حالت برای انجام عملکرد فوق طراحی گردد)

در طراحی برای سادگی در ارزیابی ماژول فرکانس و baudrate به نحو زیر در نظر گرفته شد

Freq: 100 MHZ

Baudrate: 115200

Pulse for each bit: 868

Universal Asynchronous Receiver/Transmitter


UART

Why use a UART?

- A UART may be used when:
 - High speed is not required
 - A cheap communication line between **two** devices is required
- Asynchronous serial communication is very cheap
 - Requires a transmitter and/or receiver
 - Single wire for each direction (plus ground wire)
 - Relatively simple hardware
 - Asynchronous because the
- PC devices such as mice and modems used to often be asynchronous serial devices


UART Uses

 - PC serial port is a UART!
- Serializes data to be sent over serial cable
 - De-serializes received data




UART Uses

 - Communication between distant computers
 - Serializes data to be sent to modem
 - De-serializes data received from modem




 - Used to be commonly used for internet access



UART Uses

 - Used to be used for mainframe access
 - A mainframe could have dozens of serial ports




- Becoming much less common
- Largely been replaced by faster, more sophisticated interfaces
 - PCs: USB (peripherals), Ethernet (networking)
 - Chip to chip: I2C, SPI
- Still used today when simple low speed communication is needed

UART Functions

- Outbound data
 - Convert from parallel to serial
 - Add start and stop delineators (bits)
 - Add parity bit
- Inbound data
 - Convert from serial to parallel
 - Remove start and stop delineators (bits)
 - Check and remove parity bit


UART Character Transmission

 - Below is a timing diagram for the transmission of a single byte
- Uses a single wire for transmission
- Each block represents a bit that can be a **mark** (logic '1', high) or **space** (logic '0', low)




UART Character Transmission

 - Each bit has a fixed time duration determined by the transmission rate
- Example: a 1200 bps (bits per second) UART will have a $1/1200$ s or about $833.3 \mu\text{s}$ bit width




UART Character Transmission

 - The **start bit** marks the beginning of a new word
- When detected, the receiver synchronizes with the new data stream




UART Character Transmission

 - Next follows the **data bits** (7 or 8)
- The least significant bit is sent first




UART Character Transmission

 - The **parity bit** is added to make the number of 1's even (even parity) or odd (odd parity)
- This bit can be used by the receiver to check for transmission errors




UART Character Transmission

 - The **stop bit** marks the end of transmission
- Receiver checks to make sure it is '1'
- Separates one word from the start bit of the next word




UART Character Transmission

 - In the configuration shown, it takes 10 bits to send 7 bits of data




UART Transmission Example

- Send the ASCII letter 'W' (1010111)

 

UART Character Reception

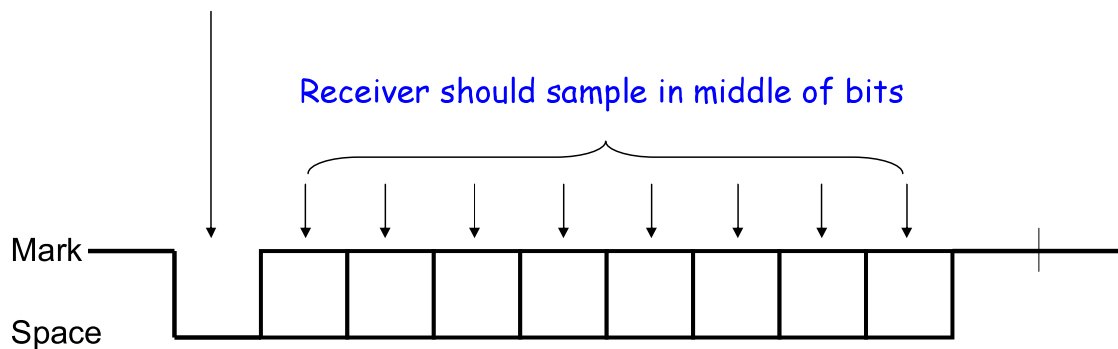
Start bit says a character is coming,
receiver resets its timers



Receiver uses a timer (counter) to time when it samples.
Transmission rate (i.e., bit width) must be known!


UART Character Reception

 If receiver samples too quickly, see what happens...



UART Character Reception

 If receiver samples too slowly, see what happens...



Receiver resynchronizes on every start bit.
Only has to be accurate enough to read 9 bits.

UART Character Reception

- Receiver also verifies that stop bit is '1'
 - If not, reports "framing error" to host system
- New start bit can appear immediately after stop bit
 - Receiver will resynchronize on each start bit

UART Options

- UARTs usually have programmable options:
 - **Data:** 7 or 8 bits
 - **Parity:** even, odd, none, mark, space
 - **Stop bits:** 1, 1.5, 2
 - **Baud rate:** 300, 1200, 2400, 4800, 9600, 19.2K, 38.4k, 57.6k, 115.2k...

```

1  -- Engineer: Mohammad Niknam
2  -- Project Name:  UART_Controller
3  library IEEE;
4  use IEEE.STD_LOGIC_1164.ALL;
5  use IEEE.NUMERIC_STD.ALL;
6
7  entity UART_RX is
8      Generic(CLK_PULSE_NUM : integer := 868); --868 for freq=100Mhz / BUADRATE 115200
9      port (   CLK : in std_logic;
10             nRST :in std_logic;
11             DATA_OUT : out std_logic_vector(7 downto 0);
12             DATA_VLD : out std_logic; -- when DATA_VLD = 1, data reception is
13             RX_Busy : out std_logic; --data reception in progress
14             Received_serial : in std_logic);
15 end UART_RX;
16
17 architecture Behavioral of UART_RX is
18     type FSMTYPE is (INIT_STATE, START_BIT_Receive, BIT_0, BIT_1, BIT_2, BIT_3, BIT_4,
19                     BIT_5, BIT_6, BIT_7, STOP_BIT_Receive);
20
21     signal CSTATE, NSTATE : FSMTYPE;
22     signal CLK_CNT : unsigned(11 downto 0) ;
23     signal CLK_CNT_RST : std_logic;
24     signal DATA_REG : std_logic_vector(7 downto 0);
25     signal TMP : std_logic_vector(7 downto 0);
26     signal DATA_VALID : std_logic;
27
28 begin
29     data_registration : process( CLK )
30         variable VTMP : std_logic_vector(7 downto 0);
31     begin
32         if (CLK'event and CLK = '1') then
33             TMP <= DATA_REG;
34             if (DATA_VALID = '1') then
35                 DATA_OUT <= DATA_REG;
36                 DATA_VLD <= '1';
37                 VTMP := DATA_REG;
38             else
39                 DATA_VLD <= '0';
40                 DATA_OUT <= VTMP;
41             end if ;
42         end if ;
43     end process ; --data_registration
44
45     clk_counter : process( CLK )
46     begin
47         if (CLK'event and CLK = '1') then
48             if (CLK_CNT_RST = '1') then
49                 CLK_CNT <= (others => '0');
50             else
51                 CLK_CNT <= CLK_CNT + 1;
52             end if ;
53         end if ;
54     end process ; -- clk_counter
55
56     state_registration : process( CLK )
57     begin
58         if (CLK'event and CLK = '1') then
59             if (nRST = '0') then
60                 CSTATE <= INIT_STATE;
61             else
62                 CSTATE <= NSTATE;
63             end if ;
64         end if ;
65     end process ; -- state_registration

```

UART_RX:

VHDL CODE

```
74 next_state : process( CSTATE, CLK_CNT, DATA_REG, Received_serial, TMP)
75 begin
76     NSTATE <= CSTATE;
77     CLK_CNT_RST <= '0';
78     DATA_VALID <= '0';
79     DATA_REG <= TMP;
80
81     case( CSTATE ) is
82     when INIT_STATE =>
83         DATA_REG <= (others => '0');
84         RX_Busy <= '0';
85         CLK_CNT_RST <= '1';
86         if (Received_serial = '0') then
87             NSTATE <= START_BIT_Receive;
88         end if ;
89
90     when START_BIT_Receive =>
91         RX_Busy <= '1';
92         if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
93             CLK_CNT_RST <= '1';
94             NSTATE <= BIT_0 ;
95         end if ;
96
97     when BIT_0 =>
98         DATA_REG(0) <= Received_serial;
99         RX_Busy <= '1';
100         if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
101             CLK_CNT_RST <= '1';
102             NSTATE <= BIT_1;
103         end if;
104
105     when BIT_1 =>
106         DATA_REG(1) <= Received_serial;
107         RX_Busy <= '1';
108         if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
109             CLK_CNT_RST <= '1';
110             NSTATE <= BIT_2;
111         end if;
112
113     when BIT_2 =>
114         DATA_REG(2) <= Received_serial;
115         RX_Busy <= '1';
116         if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
117             CLK_CNT_RST <= '1';
118             NSTATE <= BIT_3;
119         end if;
120
121     when BIT_3 =>
122         DATA_REG(3) <= Received_serial;
123         RX_Busy <= '1';
124         if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
125             CLK_CNT_RST <= '1';
126             NSTATE <= BIT_4;
127         end if;
128
129     when BIT_4 =>
130         DATA_REG(4) <= Received_serial;
131         RX_Busy <= '1';
132         if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
133             CLK_CNT_RST <= '1';
134             NSTATE <= BIT_5;
135         end if;
136
137     when BIT_5 =>
138         DATA_REG(5) <= Received_serial;
139         RX_Busy <= '1';
140         if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
141             CLK_CNT_RST <= '1';
142             NSTATE <= BIT_6;
143         end if;
144
```

```
151     when BIT_6 =>
152         DATA_REG(6) <= Received_serial;
153         RX_Busy <= '1';
154         if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
155             CLK_CNT_RST <= '1';
156             NSTATE <= BIT_7;
157         end if;
158
159     when BIT_7 =>
160         DATA_REG(7) <= Received_serial;
161         RX_Busy <= '1';
162         if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
163             CLK_CNT_RST <= '1';
164             NSTATE <= STOP_BIT_Receive;
165         end if;
166
167     when STOP_BIT_Receive =>
168         RX_Busy <= '1';
169         if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
170             CLK_CNT_RST <= '1';
171             NSTATE <= INIT_STATE;
172             RX_Busy <= '0';
173             if (Received_serial = '1') then
174                 DATA_VALID <= '1';
175             end if ;
176         end if;
177
178     when others =>
179         end case ;
180 end process ; -- next_state
181
182 end Behavioral;
```


```
1  -- Engineer: Mohammad Niknam
2  -- Project Name:  UART_Controller
3  -- VHDL Test Bench Created by ISE for module: UART_RX
4  -- CLK_PULSE_NUM : 868 for freq=100Mhz / BUADRATE 115200
5  LIBRARY ieee;
6  USE ieee.std_logic_1164.ALL;
7  use IEEE.NUMERIC_STD.ALL;
8
9  ENTITY UART_RX_TB IS
10 END UART_RX_TB;
11
12 ARCHITECTURE behavior OF UART_RX_TB IS
13
14     -- Component Declaration for the Unit Under Test (UUT)
15
16     COMPONENT UART_RX
17     PORT(
18         CLK : IN  std_logic;
19         nRST : IN  std_logic;
20         DATA_OUT : OUT std_logic_vector(7 downto 0);
21         DATA_VLD : OUT std_logic;
22         RX_Busy : OUT std_logic;
23         Received_serial : IN std_logic
24     );
25     END COMPONENT;
26
27
28     --Inputs
29     signal CLK : std_logic := '0';
30     signal nRST : std_logic := '0';
31     signal Received_serial : std_logic := '0';
32
33     --Outputs
34     signal DATA_OUT : std_logic_vector(7 downto 0);
35     signal DATA_VLD : std_logic;
36     signal RX_Busy : std_logic;
37
38     -- Clock period definitions
39     constant CLK_TIME : time := 5 ns;          --DATA_Receive_period : ((868*2)+1) *
40     CLK_TIME ns;
41
42 BEGIN
43
44     -- Instantiate the Unit Under Test (UUT)
45     uut: UART_RX PORT MAP (
46         CLK => CLK,
47         nRST => nRST,
48         DATA_OUT => DATA_OUT,
49         DATA_VLD => DATA_VLD,
50         RX_Busy => RX_Busy,
51         Received_serial => Received_serial
52     );
53
54
55
56
```

```
74 CLK <= not(CLK) after CLK_TIME;
75 nRST <= '0', '1' after 400 ns; -- hold reset state for 400 ns.
76 pro: process
77 begin
78     Received_serial <= '1';
79     wait for 5000 ns;
80     Received_serial <= '0'; --START_BIT
81     wait for 1737 * CLK_TIME;
82     Received_serial <= '0'; --BIT_0
83     wait for 1737 * CLK_TIME;
84     Received_serial <= '1'; --BIT_1
85     wait for 1737 * CLK_TIME;
86     Received_serial <= '0'; --BIT_2
87     wait for 1737 * CLK_TIME;
88     Received_serial <= '1'; --BIT_3
89     wait for 1737 * CLK_TIME;
90     Received_serial <= '0'; --BIT_4
91     wait for 1737 * CLK_TIME;
92     Received_serial <= '1'; --BIT_5
93     wait for 1737 * CLK_TIME;
94     Received_serial <= '0'; --BIT_6
95     wait for 1737 * CLK_TIME;
96     Received_serial <= '1'; --BIT_7
97     wait for 1737 * CLK_TIME;
98     Received_serial <= '1'; --STOP_BIT
99     wait for 50000 ns;
100    Received_serial <= '0'; --START_BIT
101    wait for 1737 * CLK_TIME;
102    Received_serial <= '1'; --BIT_0
103    wait for 1737 * CLK_TIME;
104    Received_serial <= '0'; --BIT_1
105    wait for 1737 * CLK_TIME;
106    Received_serial <= '1'; --BIT_2
107    wait for 1737 * CLK_TIME;
108    Received_serial <= '0'; --BIT_3
109    wait for 1737 * CLK_TIME;
110    Received_serial <= '1'; --BIT_4
111    wait for 1737 * CLK_TIME;
112    Received_serial <= '0'; --BIT_5
113    wait for 1737 * CLK_TIME;
114    Received_serial <= '1'; --BIT_6
115    wait for 1737 * CLK_TIME;
116    Received_serial <= '0'; --BIT_7
117    wait for 1737 * CLK_TIME;
118    Received_serial <= '1'; --STOP_BIT
119    wait;
120 end process;
121 END;
122
```


UART_RX Simulation:



UART_RX Simulation:

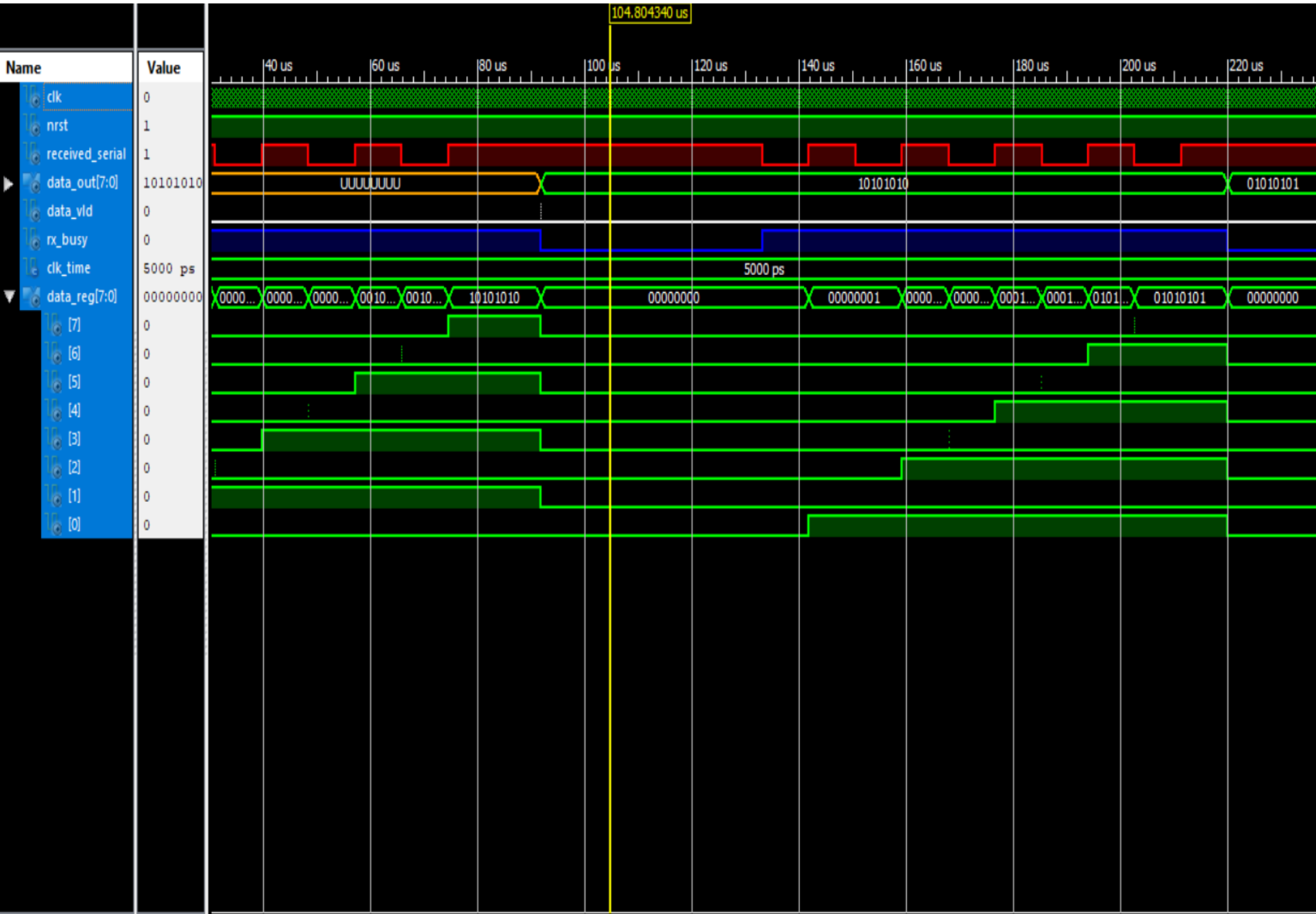

UART_RX Synthesize & RTL Schematic:

UART_RX

CLK

nRST

Received_serial

DATA_VLD


RX_Busy

DATA_OUT(7:0)


UART_RX




UART_RX Synthesize & RTL Schematic:

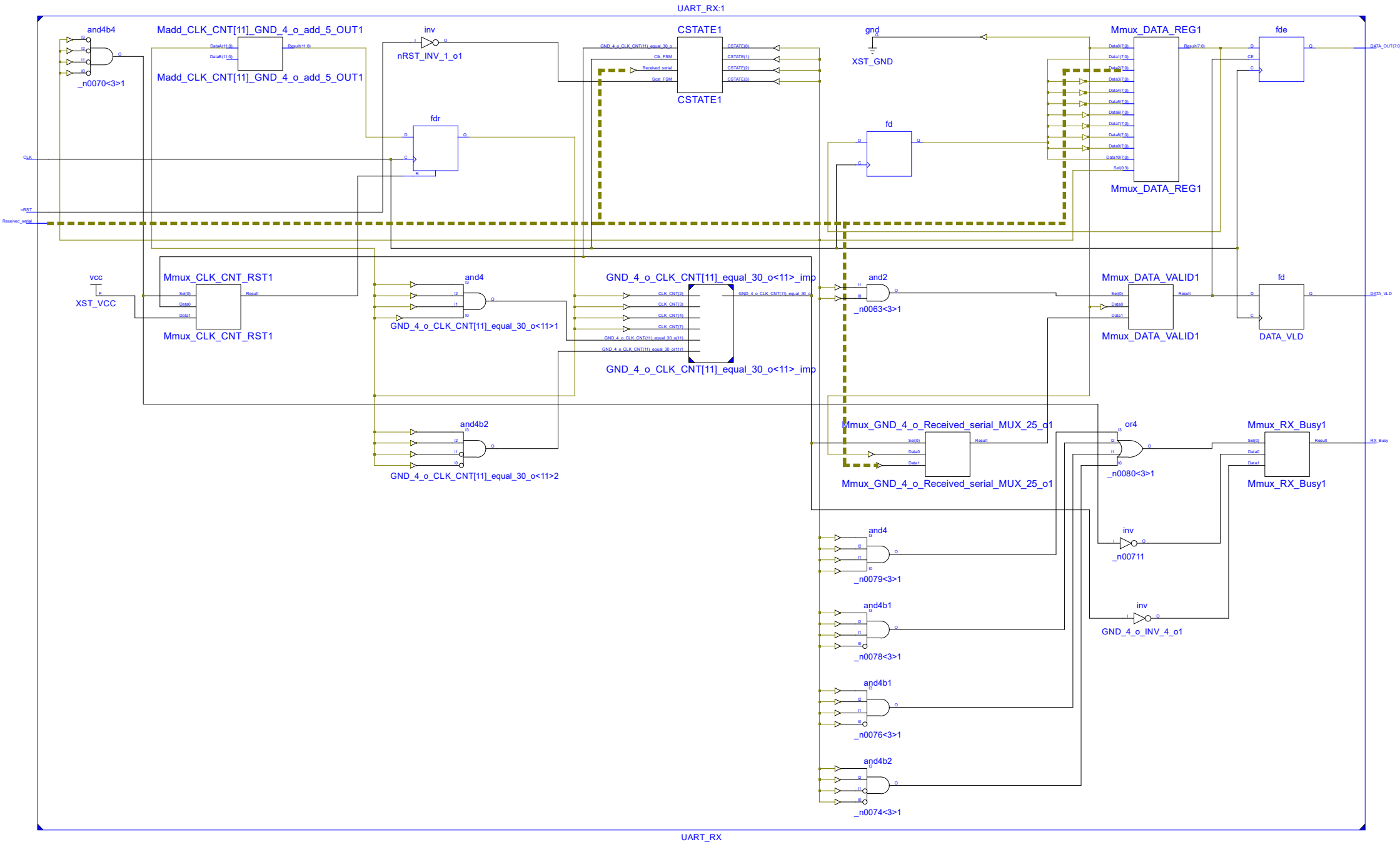

UART_RX Post-Route Simulation:

 

UART_RX Technology Schematic:

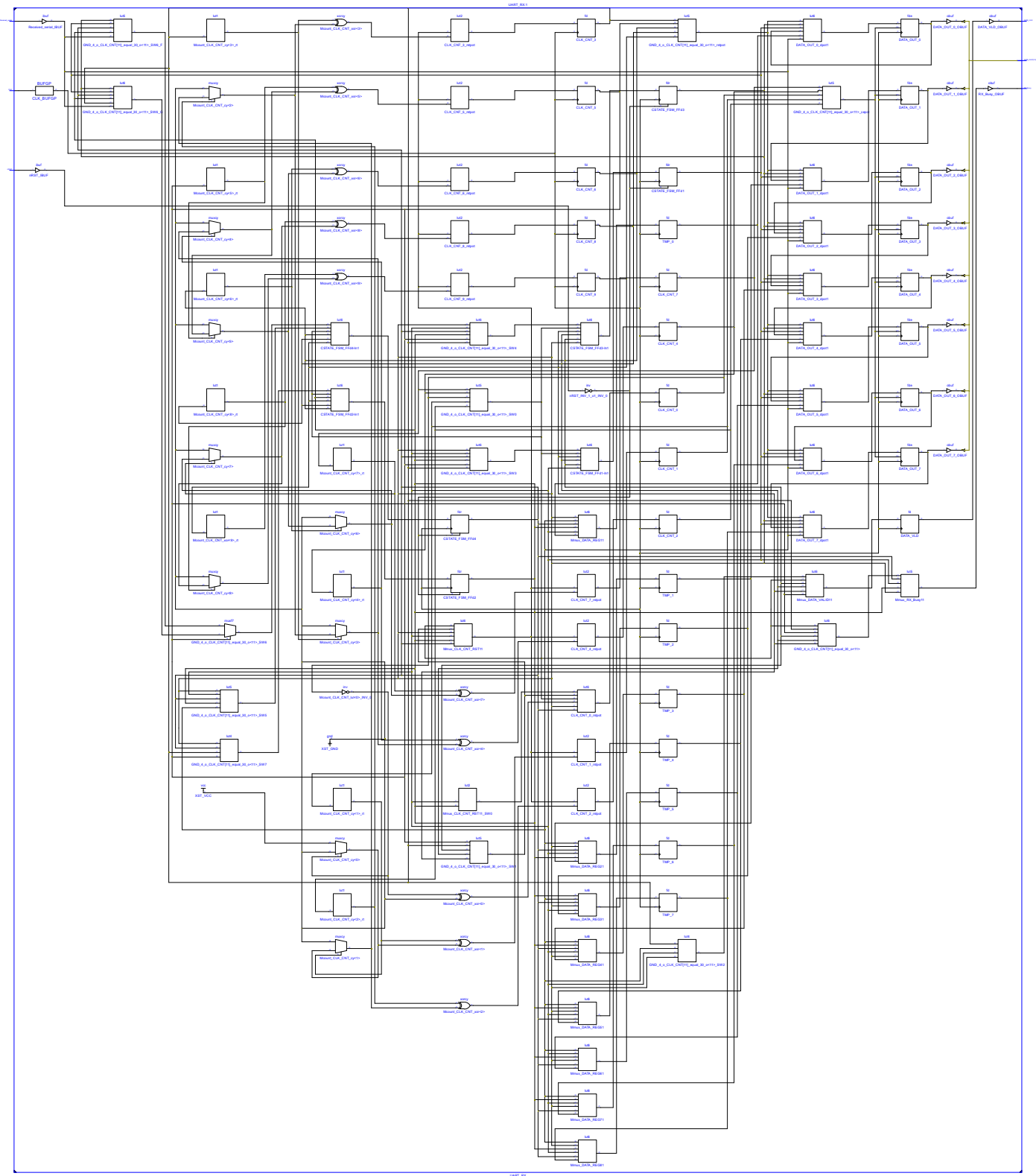

UART_TX:

VHDL CODE

```
1  -- Engineer: Mohammad Niknam
2  -- Project Name:  UART_Controller
3  -- Module Name:   UART_TX - Behavioral
4  library IEEE;
5  use IEEE.STD_LOGIC_1164.ALL;
6  use IEEE.NUMERIC_STD.ALL;
7
8  entity UART_TX is
9      Generic(CLK_PULSE_NUM : integer := 868); --868 for freq=100Mhz / BUADRATE 115200
10     port ( CLK : in std_logic;
11            nRST : in std_logic;
12            nSTART : in std_logic;
13            DATA : in std_logic_vector(7 downto 0);
14            DONE : out std_logic;
15            TX_Busy : out std_logic; --data sending in progress
16            TX : out std_logic);
17 end UART_TX;
18
19 architecture Behavioral of UART_TX is
20     type FSMTYPE is (INIT_STATE, START_BIT_SEND, BIT_0, BIT_1, BIT_2, BIT_3, BIT_4,
21                     BIT_5, BIT_6, BIT_7, STOP_BIT_SEND);
22     signal CSTATE, NSTATE : FSMTYPE;
23     signal CLK_CNT : unsigned(11 downto 0) ;
24     signal CLK_CNT_RST : std_logic;
25     signal DATA_REG : std_logic_vector(7 downto 0);
26
27 begin
28
29     data_registration : process( CLK )
30     begin
31         if (CLK'event and CLK = '1') then
32             if (nSTART = '0') then
33                 DATA_REG <= DATA;
34             end if ;
35         end if ;
36     end process ; --data_registration
37
38
39     clk_counter : process( CLK )
40     begin
41         if (CLK'event and CLK = '1') then
42             if (CLK_CNT_RST = '1') then
43                 CLK_CNT <= (others => '0');
44             else
45                 CLK_CNT <= CLK_CNT + 1;
46             end if ;
47         end if ;
48     end process ; -- clk_counter
49
50
51     state_registration : process( CLK )
52     begin
53         if (CLK'event and CLK = '1') then
54             if (nRST = '0') then
55                 CSTATE <= INIT_STATE;
56             else
57                 CSTATE <= NSTATE;
58             end if ;
59         end if ;
60     end process ; -- state_registration
61
62
```

```

74  next_state : process( CSTATE, CLK_CNT, DATA_REG, nSTART )
75  begin
76      NSTATE <= CSTATE;
77      CLK_CNT_RST <= '0';
78      TX <= '1';
79      DONE <= '0';
80
81      case( CSTATE ) is
82          when INIT_STATE =>
83              TX <= '1';
84              CLK_CNT_RST <= '1';
85              TX_Busy <= '0';
86              if (nSTART = '0') then
87                  NSTATE <= START_BIT_SEND;
88              end if ;
89
90          when START_BIT_SEND =>
91              TX <= '0';
92              TX_Busy <= '1';
93              if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
94                  CLK_CNT_RST <= '1';
95                  NSTATE <= BIT_0 ;
96              end if ;
97
98          when BIT_0 =>
99              TX <= DATA_REG(0);
100             TX_Busy <= '1';
101             if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
102                 CLK_CNT_RST <= '1';
103                 NSTATE <= BIT_1;
104             end if;
105
106          when BIT_1 =>
107              TX <= DATA_REG(1);
108              TX_Busy <= '1';
109              if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
110                  CLK_CNT_RST <= '1';
111                  NSTATE <= BIT_2;
112              end if;
113
114          when BIT_2 =>
115              TX <= DATA_REG(2);
116              TX_Busy <= '1';
117              if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
118                  CLK_CNT_RST <= '1';
119                  NSTATE <= BIT_3;
120              end if;
121
122          when BIT_3 =>
123              TX <= DATA_REG(3);
124              TX_Busy <= '1';
125              if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
126                  CLK_CNT_RST <= '1';
127                  NSTATE <= BIT_4;
128              end if;
129
130          when BIT_4 =>
131              TX <= DATA_REG(4);
132              TX_Busy <= '1';
133              if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
134                  CLK_CNT_RST <= '1';
135                  NSTATE <= BIT_5;
136              end if;
137


```


UART_TX:


VHDL CODE

```
148     when BIT_5 =>
149         TX <= DATA_REG(5);
150         TX_Busy <= '1';
151         if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
152             CLK_CNT_RST <= '1';
153             NSTATE <= BIT_6;
154         end if;
155
156     when BIT_6 =>
157         TX <= DATA_REG(6);
158         TX_Busy <= '1';
159         if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
160             CLK_CNT_RST <= '1';
161             NSTATE <= BIT_7;
162         end if;
163
164     when BIT_7 =>
165         TX <= DATA_REG(7);
166         TX_Busy <= '1';
167         if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
168             CLK_CNT_RST <= '1';
169             NSTATE <= STOP_BIT_SEND;
170         end if;
171
172     when STOP_BIT_SEND =>
173         TX <= '1';
174         TX_Busy <= '1';
175         if (to_integer(CLK_CNT) = (CLK_PULSE_NUM - 1)) then
176             CLK_CNT_RST <= '1';
177             NSTATE <= INIT_STATE;
178             DONE <= '1';
179             TX_Busy <= '0';
180         end if;
181
182     when others =>
183         end case ;
184 end process ; -- next_state
185
186 end Behavioral;
187
188
```


UART_TX Synthesize & RTL Schematic:

 

UART_TX Synthesize & RTL Schematic:

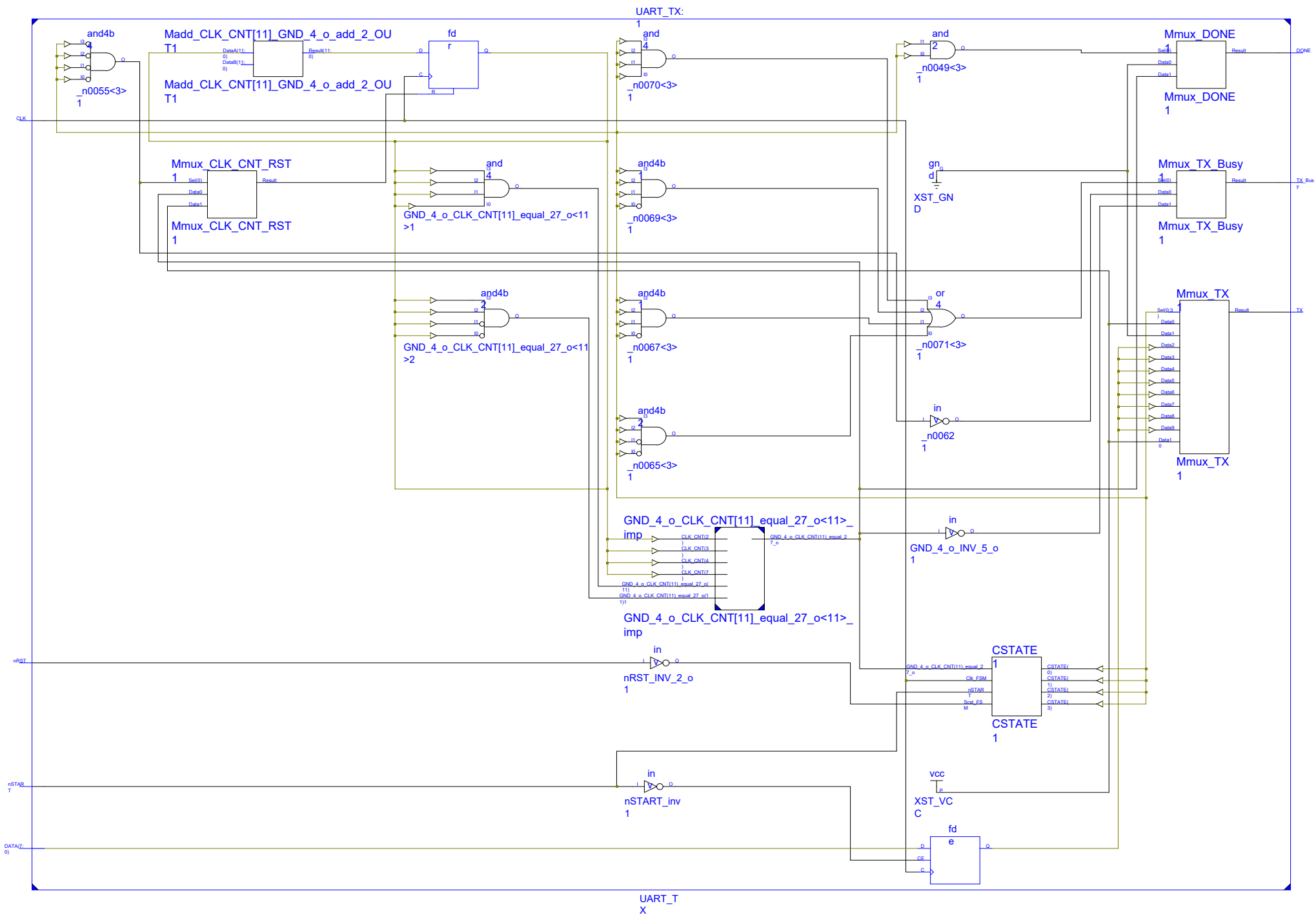

UART_TX Technology Schematic:

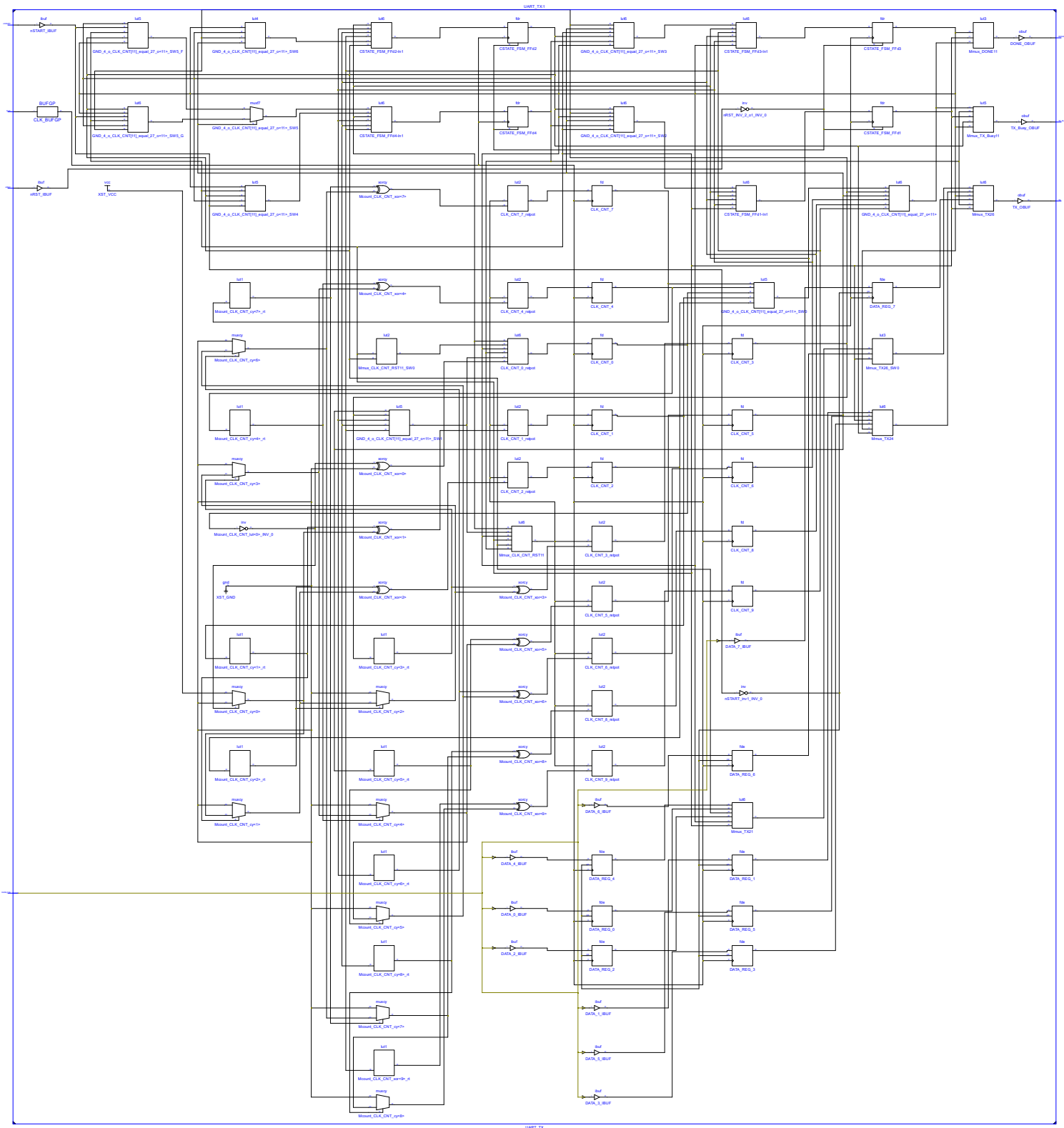


RAM_1024X8:

VHDL CODE

```
1  -- Engineer: Mohammad Niknam
2  -- Project Name:  UART Controller
3  -- Module Name:   RAM_1024X8 - Behavioral
4  library IEEE;
5  use IEEE.STD_LOGIC_1164.ALL;
6  use IEEE.NUMERIC_STD.ALL;
7
8  entity RAM_1024X8 is
9      port (
10         CLK : IN std_logic; --Clock Pulse
11         nRST :in std_logic;
12         EN : IN std_logic; --RAM Enable
13         WRITE_EN : IN std_logic; --Write Enable
14         ADDRESS : IN std_logic_vector(9 downto 0); --Address BUS for 1024 byte
15         DIN : IN std_logic_vector(7 downto 0); --Input Data
16         DOUT : OUT std_logic_vector(7 downto 0));
17 end RAM_1024X8;
18
19 architecture Behavioral of RAM_1024X8 is
20     type MEMORY_TYP is array (integer range<>) of std_logic_vector(7 downto 0);
21     signal MEM : MEMORY_TYP(0 to 1023);
22 begin
23
24     read_or_write: process(clk)
25     begin
26         if (CLK'event and CLK = '1') then
27             if (nRST='0') then
28                 if (EN='1') then
29                     if (WRITE_EN='1') then
30                         MEM(to_integer(unsigned(ADDRESS))) <= DIN;
31                     else
32                         DOUT <= MEM(to_integer(unsigned(ADDRESS)));
33                     end if;
34                 end if;
35             else
36                 MEM <= (others => "00000000");
37             end if;
38         end if;
39     end process read_or_write;
40 end Behavioral;
41
42
```

RAM_1024X8 Synthesize & RTL Schematic:

RAM_1024X8

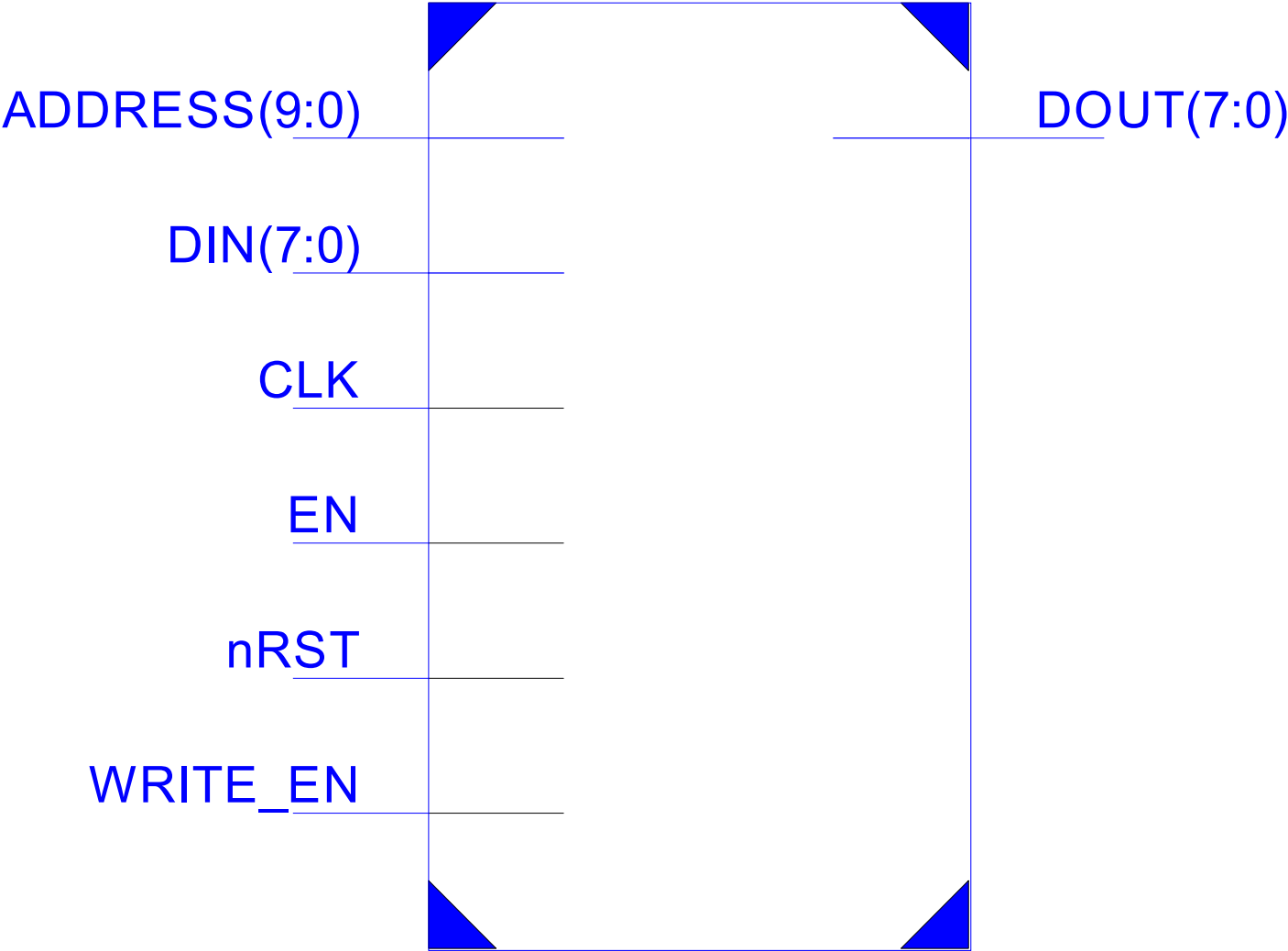

RAM_1024X8

UART_Controller:

VHDL CODE

```
1  -- Engineer: Mohammad Niknam
2  -- Project Name:  UART_Controller
3  -- Module Name:   UART_Controller - Behavioral
4
5  library IEEE;
6  use IEEE.STD_LOGIC_1164.ALL;
7  use IEEE.NUMERIC_STD.ALL;
8
9  entity UART_Controller is
10     port ( CLK : in std_logic;
11            nRST : in std_logic;
12            Serial_Receiver : in std_logic;
13            RX_Busy : out std_logic; --data reception in progress
14            Serial_Sender : out std_logic
15            );
16 end UART_Controller;
17
18 architecture Behavioral of UART_Controller is
19
20     component UART_RX
21         Generic(CLK_PULSE_NUM : integer := 868); --868 for freq=100Mhz / BUADRATE 115200
22         port ( CLK : in std_logic;
23                nRST : in std_logic;
24                DATA_OUT : out std_logic_vector(7 downto 0);
25                DATA_VLD : out std_logic; -- when DATA_VLD = 1, data reception is
26                RX_Busy : out std_logic; --data reception in progress
27                Received_serial : in std_logic);
28     end component;
29
30     component UART_TX is
31         Generic(CLK_PULSE_NUM : integer := 868); --868 for freq=100Mhz / BUADRATE 115200
32         port ( CLK : in std_logic;
33                nRST : in std_logic;
34                nSTART : in std_logic;
35                DATA : in std_logic_vector(7 downto 0);
36                DONE : out std_logic;
37                TX_Busy : out std_logic; --data sending in progress
38                TX : out std_logic);
39     end component;
40
41     component RAM_1024X8 is
42         port (
43             CLK : IN std_logic; --Clock Pulse
44             nRST : in std_logic;
45             EN : IN std_logic; --RAM Enable
46             WRITE_EN : IN std_logic; --Write Enable
47             ADDRESS : IN std_logic_vector(9 downto 0); --Address BUS for 1024 byte
48             DIN : IN std_logic_vector(7 downto 0); --Input Data
49             DOUT : OUT std_logic_vector(7 downto 0));
50     end component;
51
52     type FSMTYPE is (INIT_STATE, DATA_Reception, DATA_send);
53
54     signal CSTATE, NSTATE : FSMTYPE;
55     signal nRST_signal : std_logic;
56     signal DATA_VLD, DATA_VLD_CNT_RST : std_logic;
57     signal DATA_VLD_CNT : unsigned(10 downto 0);
58     signal RAM_ADDRESS, RAM_ADDRESS_WRITE, RAM_ADDRESS_READ : std_logic_vector(9 downto 0);
59     signal SEND_DONE, SEND_DONE_CNT_RST : std_logic;
60     signal SEND_DONE_CNT : unsigned(10 downto 0);
61     signal RX_DATA_OUT, RAM_DOUT : std_logic_vector(7 downto 0);
62     signal WRITE_EN, RAM_EN : std_logic;
63     signal TX_Busy, nSTART_signal : std_logic;
```

```

73  begin
74      DATA_VLD_counter_AND_SEND_DONE_counter : process( CLK )
75      begin
76          if (CLK'event and CLK = '1') then
77              if (DATA_VLD_CNT_RST = '1') then
78                  DATA_VLD_CNT <= (others => '0');
79                  RAM_EN <= '0';
80              else
81                  if (DATA_VLD = '1') then
82                      DATA_VLD_CNT <= DATA_VLD_CNT + 1;
83                      RAM_EN <= '1';
84                  else
85                      RAM_EN <= '0';
86                  end if;
87              end if ;
88
89              if (SEND_DONE_CNT_RST = '1') then
90                  SEND_DONE_CNT <= (others => '0');
91              else
92                  if (SEND_DONE = '1') then
93                      SEND_DONE_CNT <= SEND_DONE_CNT + 1;
94                      RAM_EN <= '1';
95                  else
96                      RAM_EN <= '0';
97                  end if;
98              end if ;
99          end if ;
100      end process ; -- DATA_VLD_counter_AND_SEND_DONE_counter
101
102
103      RAM_ADDRESS_WRITE_PRO: process(CLK, DATA_VLD_CNT)
104          variable DATA_VLD_CNT_var : unsigned(10 downto 0);
105      begin
106          DATA_VLD_CNT_var := DATA_VLD_CNT + "1111111111";    --DATA_VLD_CNT Minus One
107          to address
108          RAM_ADDRESS_WRITE <= std_logic_vector(DATA_VLD_CNT_var(9 downto 0));
109      end process RAM_ADDRESS_WRITE_PRO; --RAM_ADDRESS_WRITE_PRO
110
111      RAM_ADDRESS_READ <= std_logic_vector(SEND_DONE_CNT(9 downto 0));
112
113
114      state_registration : process( CLK )
115      begin
116          if (CLK'event and CLK = '1') then
117              if (nRST = '0') then
118                  CSTATE <= INIT_STATE;
119              else
120                  CSTATE <= NSTATE;
121              end if ;
122          end if ;
123      end process ; -- state_registration
124
125
126      next_state : process( CSTATE, RAM_ADDRESS_WRITE, RAM_ADDRESS_READ, DATA_VLD,
127                          DATA_VLD_CNT, SEND_DONE_CNT, TX_Busy)
128      begin
129          NSTATE <= CSTATE;
130          nRST_signal <= '1';
131          DATA_VLD_CNT_RST <= '0';
132          SEND_DONE_CNT_RST <= '0';
133          WRITE_EN <= '1';
134          RAM_ADDRESS <= (others => '0');
135          nSTART_signal <= '1';

```



```

143     case( CSTATE ) is
144         when INIT_STATE =>
145             nRST_signal <= '0';
146             DATA_VLD_CNT_RST <= '1';
147             SEND_DONE_CNT_RST <= '1';
148             if (DATA_VLD = '1') then
149                 NSTATE <= DATA_Reception;
150             end if ;
151
152         when DATA_Reception =>
153             WRITE_EN <= '1';
154             RAM_ADDRESS <= RAM_ADDRESS_WRITE;
155             SEND_DONE_CNT_RST <= '1';
156             if (DATA_VLD_CNT = "100000000000") then --100000000000=1024
157                 DATA_VLD_CNT_RST <= '1';
158                 NSTATE <= DATA_send ;
159             end if ;
160
161         when DATA_send =>
162             WRITE_EN <= '0';
163             RAM_ADDRESS <= RAM_ADDRESS_READ;
164             DATA_VLD_CNT_RST <= '1';
165             if (SEND_DONE_CNT = "100000000000") then --100000000000=1024
166                 SEND_DONE_CNT_RST <= '1';
167                 NSTATE <= INIT_STATE ;
168             else
169                 if (TX_Busy = '0') then
170                     nSTART_signal <= '0';
171                 else
172                     nSTART_signal <= '1';
173                 end if;
174             end if ;
175
176         when others =>
177             end case ;
178     end process ; -- next_state
179
180

```

```

181 UART_RX_Instantiation : UART_RX
182 Generic map(CLK_PULSE_NUM => 868)
183 port map(
184     CLK => CLK,
185     nRST => nRST_signal,
186     DATA_OUT => RX_DATA_OUT,
187     DATA_VLD => DATA_VLD,
188     RX_Busy => RX_Busy,
189     Received_serial => Serial_Receiver
190 );
191

```

```

192 UART_TX_Instantiation : UART_TX
193 Generic map(CLK_PULSE_NUM => 868)
194 port map(
195     CLK => CLK,
196     nRST => nRST_signal,
197     nSTART => nSTART_signal,
198     DATA => RAM_DOUT,
199     DONE => SEND_DONE,
200     TX_Busy => TX_Busy,
201     TX => Serial_Sender
202 );
203

```


```

204 RAM_1024X8_Instantiation : RAM_1024X8
205 port map(
206     CLK => CLK,
207     nRST => nRST_signal,
208     EN => RAM_EN,
209     WRITE_EN => WRITE_EN,
210     ADDRESS => RAM_ADDRESS,
211     DIN => RX_DATA_OUT,
212     DOUT => RAM_DOUT
213 );
214

```

end Behavioral;

UART_Controller

 

UART_Controller

UART_Controller Synthesize & RTL Schematic:

